

11. AC Circuit Power Analysis

11.1 Instantaneous power

◆ Resistance

$$\begin{aligned} p(t) &= v(t) \cdot i(t) \\ &= i^2(t) \cdot R \\ &= v^2(t)/R \end{aligned}$$

◆ Inductance

$$\begin{aligned} p(t) &= v(t) \cdot i(t) \\ &= L \cdot i(t) \frac{di(t)}{dt} \end{aligned}$$

◆ Capacitance

$$\begin{aligned} p(t) &= v(t) \cdot i(t) \\ &= C \cdot v(t) \frac{dv(t)}{dt} \end{aligned}$$

Example)

$$i(t) = \frac{V_0}{R} (1 - e^{-\frac{R}{L}t}) u(t)$$

total power delivered by the source

$$\begin{aligned} p(t) &= v(t) \cdot i(t) \\ &= \frac{V_0^2}{R} (1 - e^{-\frac{R}{L}t})^2 u(t) \end{aligned}$$



power delivered to (dissipated by) the R

$$\begin{aligned} p_R(t) &= i^2(t)R \\ &= \frac{V_0^2}{R} (1 - e^{-\frac{R}{L}t})^2 u(t) \end{aligned}$$

power absorbed by inductor L

$$\begin{aligned} p_L(t) &= v_L(t) \cdot i(t) \\ &= \frac{V_0^2}{R} e^{-\frac{R}{L}t} (1 - e^{-\frac{R}{L}t}) u(t) \end{aligned}$$
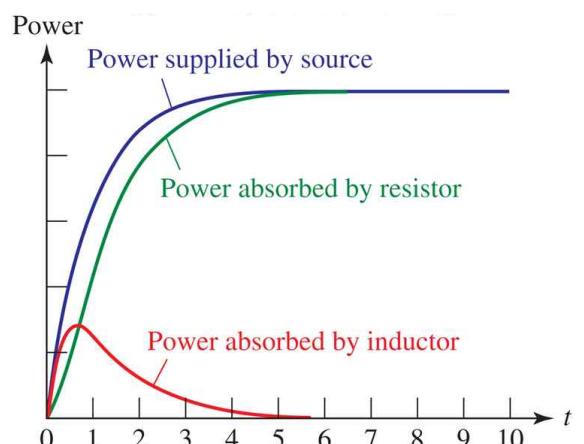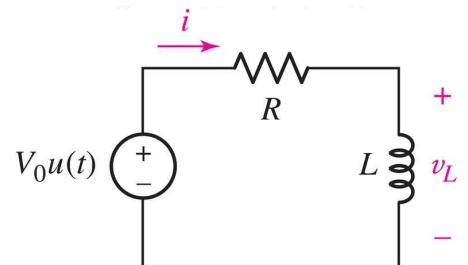
$$\text{where } v_L(t) = L \frac{di(t)}{dt} = V_0 e^{-\frac{R}{L}t} u(t)$$



11.2 Average power.

over the interval $[t_1, t_2]$,


$$P = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} p(t) dt$$

for a periodic fn.

$$f(t) = f(t + T)$$

average power over one period.
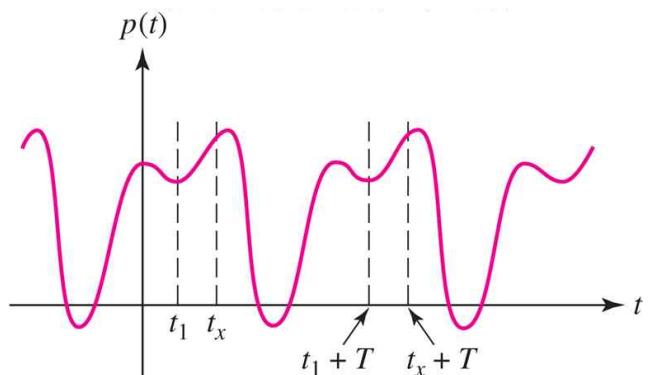
$$P = \frac{1}{T} \int_{t_1}^{t_1+T} p(t) dt$$



◆ Average power in the sinusoidal steady state.

$$v(t) = V_m \cos(\omega t + \theta) \text{ and } i(t) = I_m \cos(\omega t + \phi)$$

instantaneous power.

$$\begin{aligned} p(t) &= V_m I_m \cos(\omega t + \theta) \cos(\omega t + \phi) \\ &= \frac{1}{2} V_m I_m \cos(2\omega t + \theta + \phi) + \frac{1}{2} V_m I_m \cos(\theta - \phi) \\ &= [\text{sinusoids with twice the applied freq.}] + [\text{constant term}] \end{aligned}$$

Hence, average power.

$$P = \frac{1}{2} V_m I_m \cos(\theta - \phi)$$

Example 11.2) $v(t) = 4 \cos(\pi t / 6)$,

$$V = 4(V) \text{ and } Z = 2 \angle 60^\circ$$

Average power and instantaneous power?

sol)

Phasor current

$$I = \frac{V}{Z} = 2 \angle -60^\circ \quad \Rightarrow \quad i(t) = 2 \cos(\pi t / 6 - 60^\circ)$$

Average power

$$P = \frac{1}{2} \cdot 4 \cdot 2 \cos(0^\circ + 60^\circ) = 4 \cos(60^\circ) = 2(W)$$

instantaneous power.

$$\begin{aligned} p(t) &= 8 \cos(\pi t / 6) \cos(\pi t / 6 - 60^\circ) \\ &= 2 + 4 \cos(\pi t / 3 - 60^\circ) \end{aligned}$$

◆ Average power absorbed by Resistor

same phase (in phase)

$$v(t) = V_m \cos(\omega t + \theta) \text{ and } i(t) = I_m \cos(\omega t + \theta)$$

Average power

$$\begin{aligned} P &= \frac{1}{2} V_m I_m \cos(\theta - \theta) \\ &= \frac{1}{2} V_m I_m = \frac{1}{2} \frac{V_m^2}{R} = \frac{1}{2} I_m^2 R \end{aligned}$$

◆ Average power absorbed by Reactive elements (L and C)

phase difference : $\pm 90^\circ$

Average power


$$P = \frac{1}{2} V_m I_m \cos(\pm 90^\circ) = 0(W)$$

Example 11.3) $Z_L = 8 - j11(\Omega)$ by a current $I = 5 \angle 20^\circ (A)$

sol) $Z_L = 8 - j11(\Omega) = R + jX$ (저항 + 리액턴스)

$$\Rightarrow P = \frac{1}{2} I_m^2 R = 100(W)$$

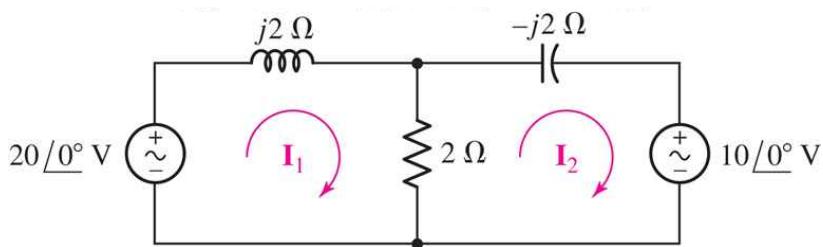Example 11.4) Average power of each elements?



sol)

$$P_L = P_C = 0(W)$$

$$\begin{aligned} I_1 &= 5 - j10 = 11.18 \angle -63.43^\circ \quad \Rightarrow \quad I_1 - I_2 = -j5 = 5 \angle -90^\circ \\ I_2 &= 5 - j5 = 7.07 \angle -45^\circ \end{aligned}$$


$$P_{2\Omega} = \frac{1}{2} I_m^2 R = 25(W)$$

$$P_{l_{source}} = \frac{1}{2} V_m I_m \cos(\theta - \phi) = \frac{1}{2} \times 20 \times (-11.18) \times \cos(63.43^\circ) = -50(W)$$

$$P_{r_{source}} = \frac{1}{2} V_m I_m \cos(\theta - \phi) = \frac{1}{2} \times 20 \times 11.18 \times \cos(45^\circ) = 25(W)$$

◆ Maximum power transfer.

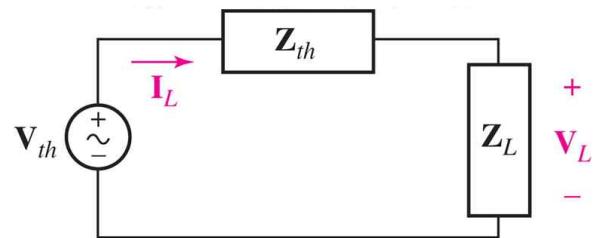The average power delivered to the load is maximum when $Z_L = Z_{th}$. (impedance matching)




11.3 Effective values of current and voltage

※ ac 110v or 220v having a freq. of 60Hz

⇒ What is meant by “110“ volts?

“Effective value” or “rms(root mean square) value”


(dc V_{eff} 와 동일한 효과의 전압을 저항에 공급)

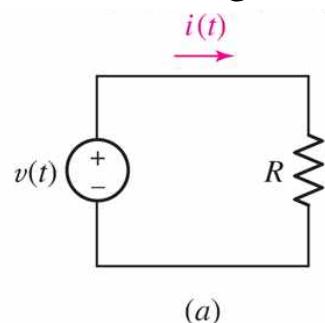

(a)

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} = V_{eff}$$
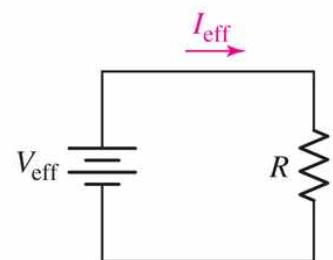
$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} = I_{eff}$$



(b)

◆ rms value of Sinusoids

$$\begin{aligned} I_{rms} &= \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} \quad \leftarrow i(t) = I_m \cos(wt + \phi) \\ &= I_m \sqrt{\frac{1}{T} \int_0^T \cos^2(wt + \phi) dt} \quad \leftarrow \cos^2(A) = [1 + \cos(2A)]/2 \\ &= I_m \sqrt{\frac{1}{2T} \int_0^T [1 + \cos(2wt + 2\phi)] dt} \\ &= I_m \sqrt{\frac{1}{2T} [T + 0]} \\ &= \frac{I_m}{\sqrt{2}} \end{aligned}$$

11.4 Apparent Power and Power Factor

Impedance Z_L applied by $v(t) = V_m \cos(\omega t + \theta)$

\Rightarrow the current $i(t) = I_m \cos(\omega t + \phi)$

Average power

$$\begin{aligned} P &= \frac{1}{2} V_m I_m \cos(\theta - \phi) \\ &= V_{eff} I_{eff} \cos(\theta - \phi) \end{aligned}$$

where apparent power is

$$P_{apparent} = V_{eff} I_{eff}$$

Power factor

$$PF = \frac{\text{Average Power}}{\text{Apparent Power}} = \cos(\theta - \phi)$$

Example 11.8) Average power, Apparent power, and Power factor?

sol)

total impedance

$$Z = 3 + j4 = 5 \angle 53.13^\circ$$

current

$$I = \frac{V}{Z} = \frac{60 \angle 0^\circ}{5 \angle 53.13^\circ} = 12 \angle -53.13^\circ$$

Average power

$$\begin{aligned} P &= \frac{1}{2} V_m I_m \cos(\theta - \phi) \\ &= V_{eff} I_{eff} \cos(\theta - \phi) \\ &= I_{eff}^2 R = 12^2 \times 3 = 432 \text{ (W)} \end{aligned}$$

Apparent power

$$P = V_{eff} I_{eff} = 60 \times 12 = 720 \text{ (W)}$$

Power factor

$$\begin{aligned} PF &= \cos(\theta - \phi) = \cos(53.13^\circ) = 0.6 \\ &= \frac{432}{720} = 0.6 \end{aligned}$$

